

# CS 2110 Lab 4

## Transistors: The building blocks of gates

Your TAs! :)

Fall 2018

### 1 Recitation Outline

1. DeMorgan's Law
2. States of a wire in CircuitSim
  - (a) Low (dark green) (0) (0 volts)
  - (b) High Impedance (blue) (undefined) (undefined voltage)
  - (c) FIRE, exclamation mark, FIRE, exclamation mark, HELP ME, exclamation mark (red) (conflicting voltages)
3. Transistors
  - (a) Essentially a very tiny switch
  - (b) Source and drain
  - (c) P type
    - i. Normally closed (current passing through)
    - ii. Connects to power
  - (d) N type
    - i. Normally open (**no** current passing through)
    - ii. Connects to ground
4. Building Boolean Circuits With Transistors
  - (a) Circuits model boolean expressions
  - (b) Fully simplify a boolean expression
  - (c) 1 (voltage) is True, 0 (ground) is False
  - (d) Transistors in series: AND
  - (e) Transistors in Parallel: OR
  - (f) Pull-up network using P types
  - (g) Pull-down network using N types (should be the negation of the pull-up network)

### 2 De-Morgan's Law

Laws for Boolean Algebra

- (not A and not B) = not (A or B)

$$\overline{A} \&\& \overline{B} = \overline{A||B}$$

- (not A or not B) = not (A and B)

$$\overline{A} || \overline{B} = \overline{A\&\&B}$$


### 3 Which switch is which?

Draw a squiggly line on the board and claim it's a wire connected to nothing. It's just sitting there. **Question for the class:** what value is on this wire?

If you said 0, you're wrong. In this class, we will consider wires to have one of three values:

- 0 (current flows from ground). Dark green in CircuitSim
- 1 (current flows from power). Light green in CircuitSim
- high impedance / floating (no current flowing). Blue in CircuitSim

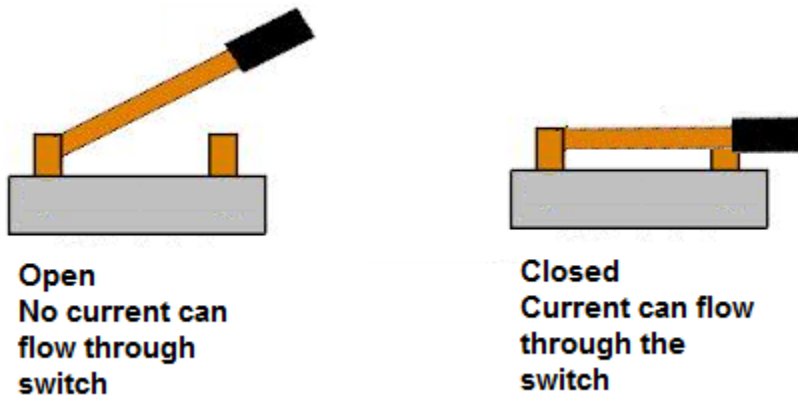
A switch either allows current to flow (from ground or power, aka 0 or 1) or prevents current from flowing (floating):



Note that when it's closed, that just means current flows. The current flowing through the switch could have a 0 or 1 value.

Now... what if we had a switch you could open or close based on the value a wire, made out of semiconductor so it's super compact? Might be useful, asking for a friend

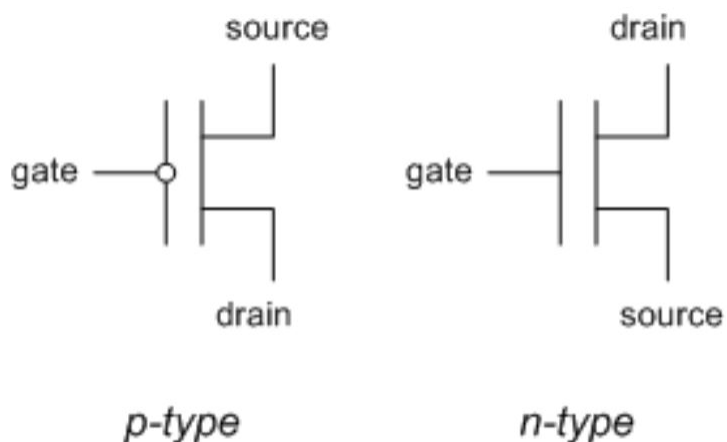
### 4 Transistors: The building blocks of gates



Each transistor has a source, drain, and gate. The input of the gate determines whether the switch will be closed, allowing current to flow from the source to the drain.

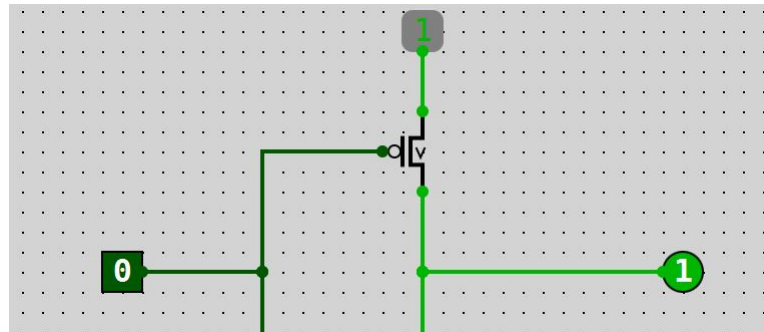
## 4.1 P-type transistors

- P-type transistors connect to Power(Voltage/logical 1).
- Whenever the gate value is '0', the p-type switch closes, allowing power to send a '1' to the output


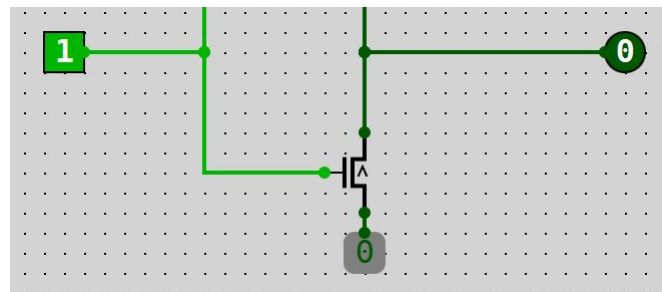
## 4.2 N-type transistors

- N-type transistors connect to Ground(No Voltage/logical 0).
- Whenever the gate value is '1', the n-type switch closes, allowing ground to send a '0' to the output



# 5 Using transistors to build circuits

## 5.1 Rules for converting from transistors to circuits

1. Begin with a fully simplified boolean expression, let's refer to this expression as F. (Ex.  $F = A \&\& B$ )
2. Expression F tells you when you want the output to be true, you want to use F to create the 'pull-up' network that is connected to the voltage.
  - Use p-type switches
  - Connect the switches in series for an 'and' network
  - Connect the switches in parallel for an 'or' network
  - Since p-type switches pull from voltage only when the input is '0', they work on the negated values of inputs.
3. F also tells you when you want the output to be false, you want to use expression F to create the 'pull-down' network that is connected to the ground
  - Use n-type switches
  - The 'pull-down' expression is the negated version of the 'pull-up' expression


The easiest way to convert from transistors to circuits is by using a simplified expression  
 Ex. NOR

1.  $F = \overline{A \parallel B}$

2. Using DeMorgan's Theorem:


(a) Pull up expression:  $\overline{A \parallel B} = \overline{A} \&\& \overline{B}$

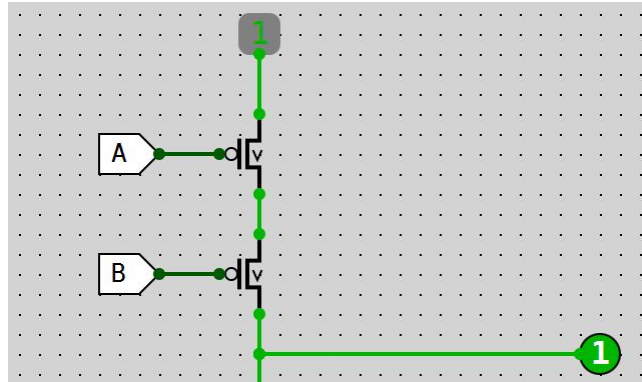(b) With the 'pull-up' network / network connected to voltage, since it is an 'and' operation, connect the complement of the inputs to the switches in series




(c) Pull down expression:  $\overline{\overline{A} \&\& \overline{B}} = A \parallel B$

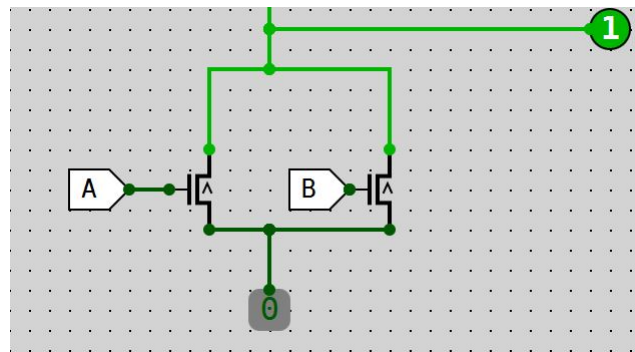(d) With the 'pull-down' network / network connected to ground, since it is an 'or' operation, connect the inputs to the switches in parallel



(e) NOR circuit using transistors

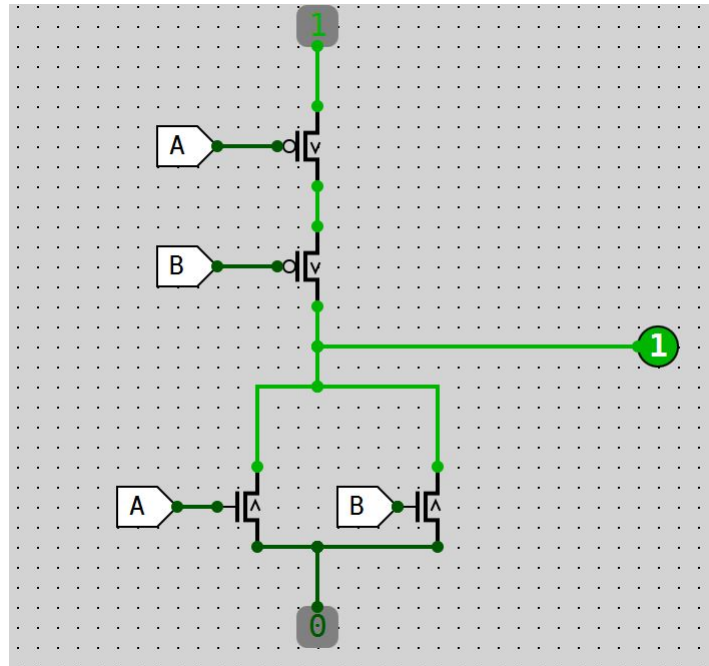

- (f) This method is a fool-safe method of creating NAND and NOR gates. For an AND or OR gate, you will need to create a NAND/NOR gate respectively and add the NOT circuitry afterwards.

## 6 Hints when making transistors in circuitsim

- Make sure the arrow of the transistor is pointed towards the output